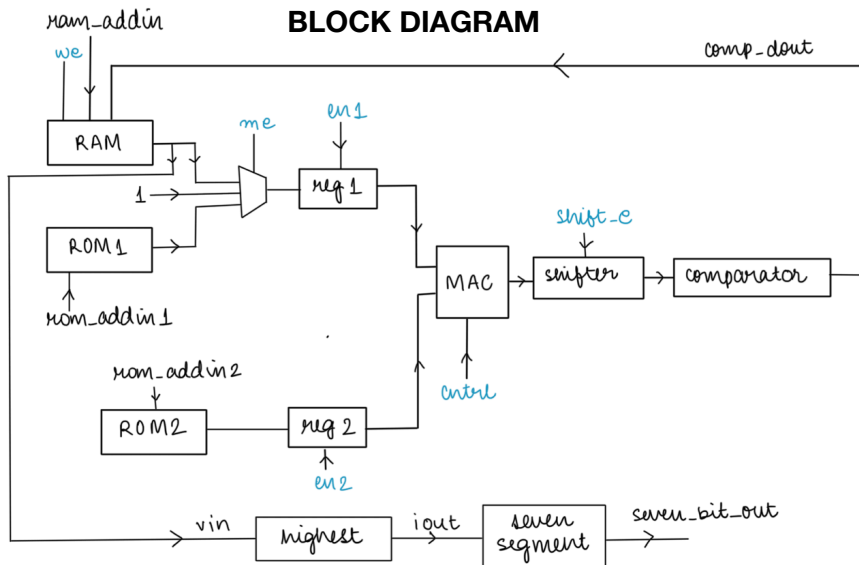


# COL 215 - Assignment 2 Part 2

## 2020CS50438 - Richa Yadav

## 2020CS50429 - Manshi Sagar

### BLOCK DIAGRAM



Blue signals - Control Path  
Black - Data Path  
Blocks (rectangles) - Components

### Additional Components :

- HIGHEST** : This component takes one element of product\_layer2 as input, compares it with the current maximum and outputs the current maximum.
- SEVEN SEGMENT** : Takes as input a 1-digit (4 bit) number and outputs the cathode and anode configuration needed to display it on the Basys3 board



$$\text{Layer 1 : } (1 \times 784) \times (784 \times 64) + (1 \times 64) \rightarrow (1 \times 64)$$

Input                      weight                      bias                      product\_layer1


$$\text{Layer 2 : } (1 \times 64) \times (64 \times 10) + (1 \times 10) \rightarrow (1 \times 10)$$

product\_layer1                      weight                      bias                      product\_layer2

### SIMULATION

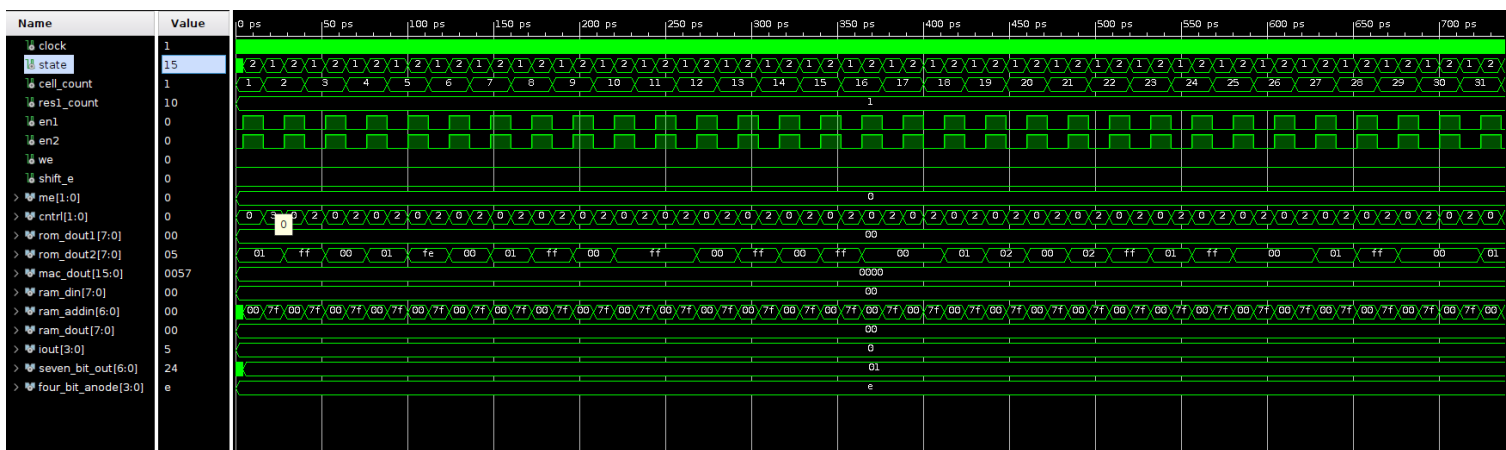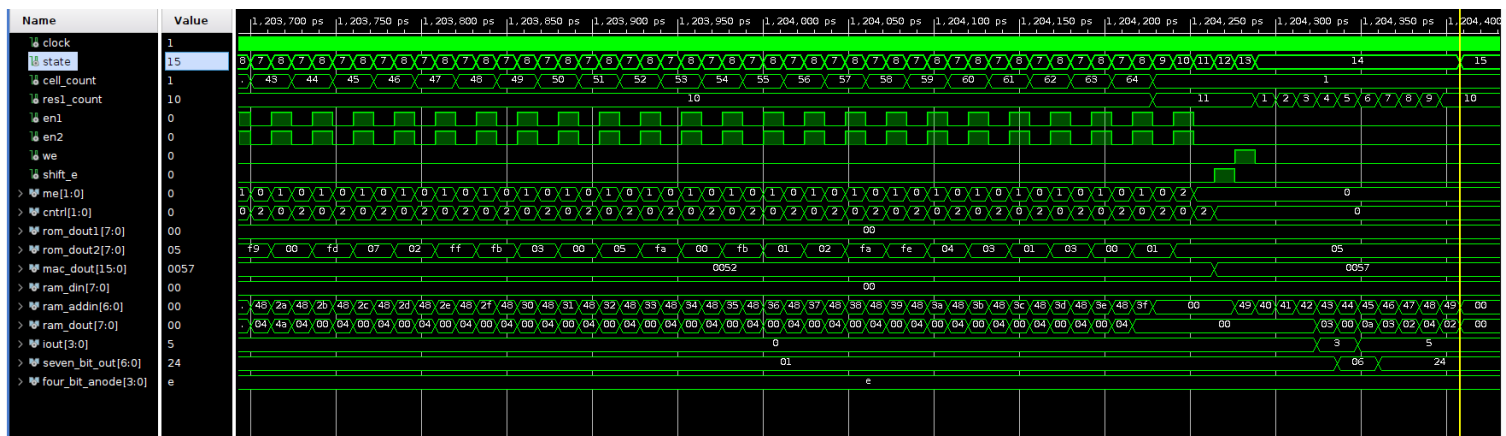

# FINITE STATE MACHINE

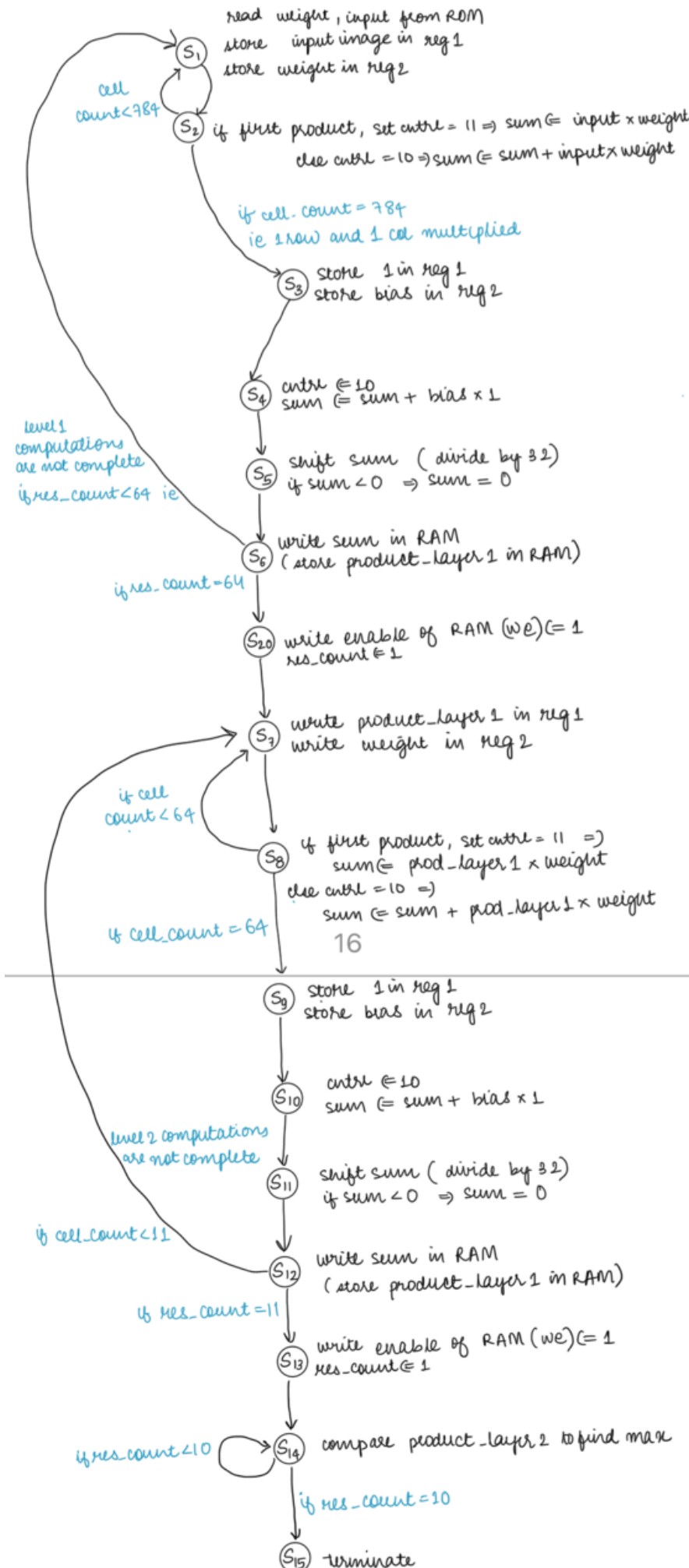

S1 to S6 := Layer 1

S7 := Write Product\_layer 1 in RAM

S7 to S12 := Layer 2

S13 := Write Product\_layer 2 in RAM

S14 := Find output class by taking maximum of Product\_layer 2